

**ECT2601
RCT2601**

May/June 2016

ELECTRONICS II (THEORY)

Duration 3 Hours

100 Marks

EXAMINERS

FIRST
SECOND

MR PO UMENNE
MR NR NETSHIKWETA

Programmable pocket calculator is permissible

Closed book examination

This examination question paper remains the property of the University of South Africa and may not be removed from the examination venue

This examination question paper consists of 9 pages including this "cover" plus 4 pages formulae sheets

Answer all questions

PLEASE NOTE: IF YOU HAVE THE OPINION THAT INSUFFICIENT INFORMATION IS SUPPLIED FOR YOU TO ANSWER A PARTICULAR QUESTION, MAKE A REALISTIC ASSUMPTION, MOTIVATE IT AND THEN ANSWER THE QUESTION.

BIPOLAR JUNCTION TRANSISTORS

Question 1

The transistor in **Figure 1** has the following maximum ratings $P_{D(max)} = 500mW$, $V_{CE(max)} = 25V$, and $I_{C(max)} = 200mA$

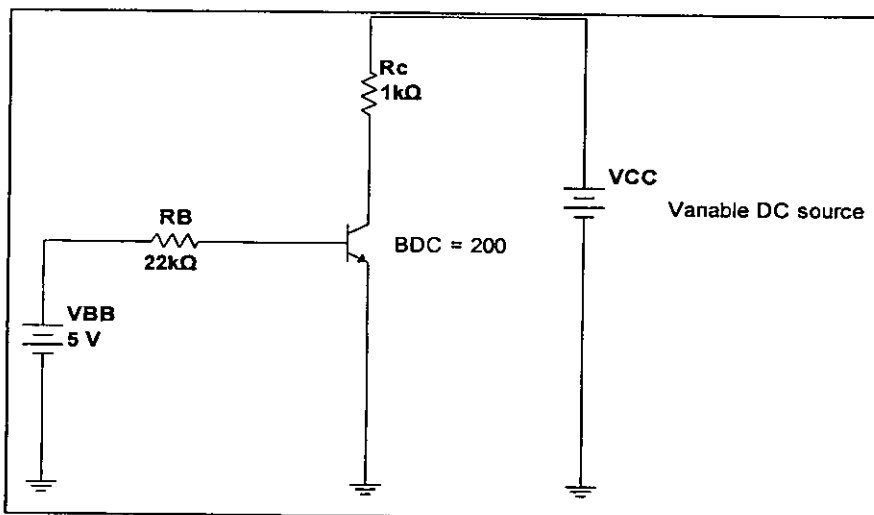


Figure 1

- 1 1 Determine the maximum value to which V_{CC} can be adjusted without exceeding a rating (8)
 - 1 2 Which rating would be exceeded first? (6)
- [14]**

[TURN OVER]

Question 2

A transistor has a $P_{D(max)} = 5W$ at $25^{\circ}C$. The derating factor is $7mW/^{\circ}C$. What is the $P_{D(max)}$ at $80^{\circ}C$?

(4)

[4]**Question 3**

A $50mV$ signal is applied to the base of a properly biased transistor with $r_e' = 10\Omega$ and $R_C = 560\Omega$. Determine the signal voltage at the collector

(4)

[4]**TRANSISTOR BIAS CIRCUITS****Question 4**

Refer to **Figure 2** to answer the following questions

4.1 Determine the Q-point for the circuit in **Figure 2** (6)

4.2 Find the maximum peak value of the base current for linear operation. Assume $B_{DC} = 250$ (6)

[TURN OVER]

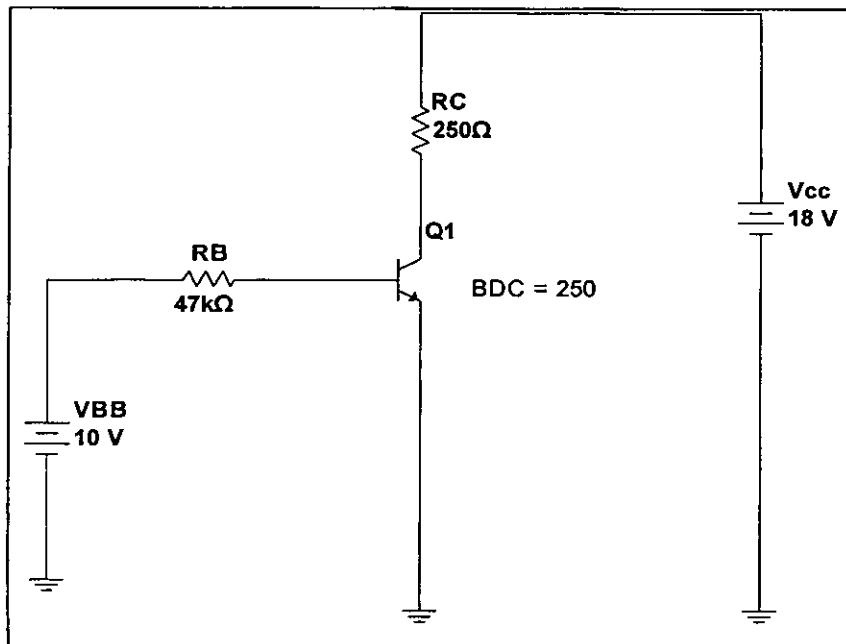


Figure 2

[12]

Question 5

For the circuit in **Figure 3** and

- 5.1 Determine the Q-point values for the transistor voltage divider circuit (6)
- 5.2 Determine the minimum power rating of the transistor (2)
- 5.3 Calculate I_1 , I_2 and I_B for the circuit in **Figure 3** (8)

[TURN OVER]

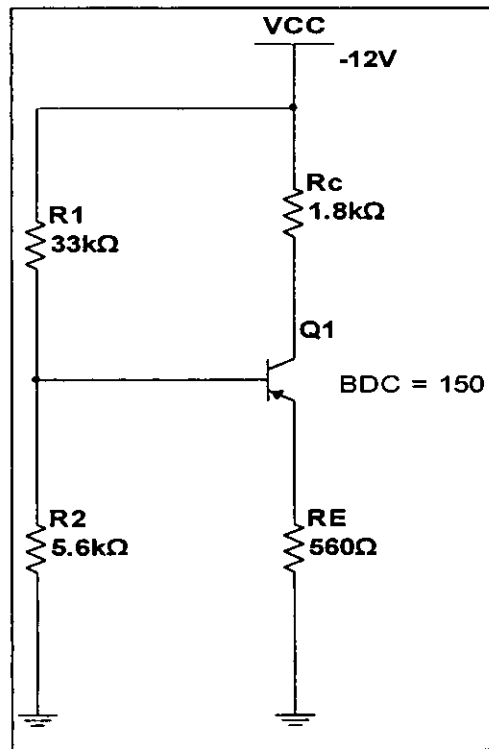


Figure 3

[16]

Question 6

For the emitter bias circuit in Figure 4, determine the correct voltages, V_B, V_E, V_C, V_{CE} at the transistor terminals with respect to ground. Assume $B_{DC} = 100$. (10)

[TURN OVER]

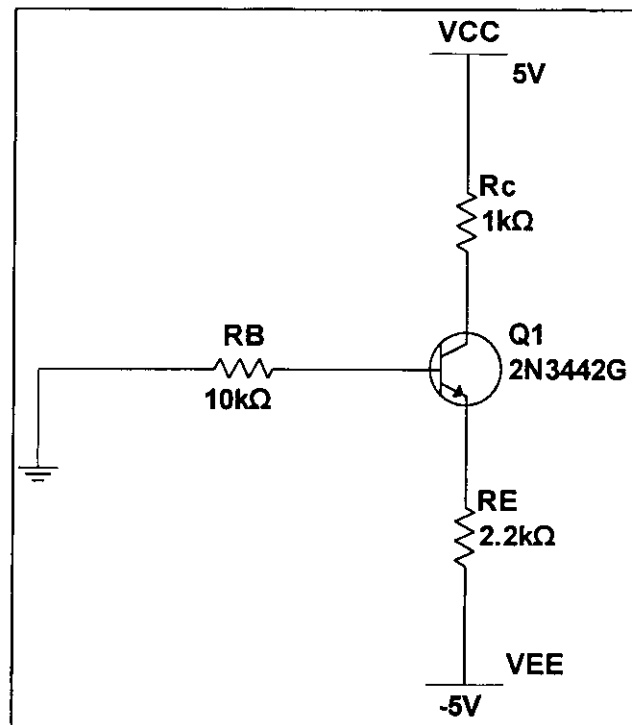


Figure 4

[10]

BJT AMPLIFIERS**Question 7**For the BJT amplifier in **Figure 5**,

- 7 1 Determine all the dc terminal voltages (10)
- 7 2 Calculate
- 7 2 1 r'_e (2)
- 7 2 2 $R_{in(base)}$ (2)
- 7 2 3 $R_{in(tot)}$ (2)

[TURN OVER]

- 7 2 4 Attenuation (2)
- 7 2 5 A_v (Voltage gain) (2)
- 7 2 6 A'_v (Overall voltage gain) (2)
- 7 2 7 The ac collector voltage V_c (2)

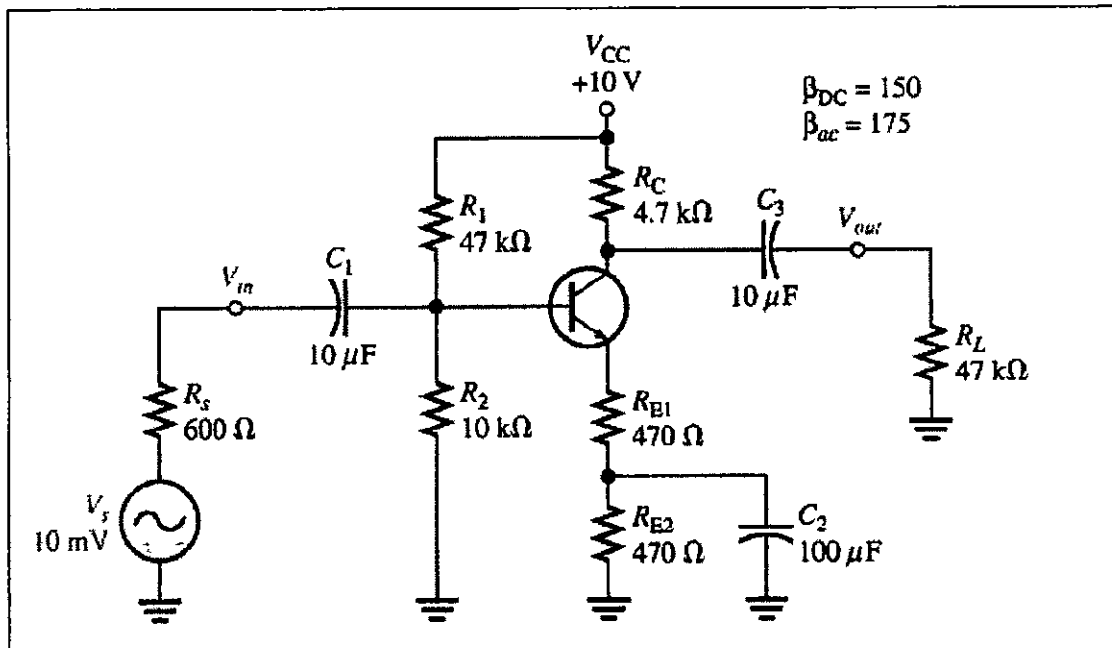


Figure 5

[24]

FIELD-EFFECT TRANSISTORS (FET's)

Question 8

- 8 1 Determine the Q-point for the JFET with voltage-divider bias in Figure 6, given that the device has a transfer characteristic curve shown in Figure 7 (10)
- 8 2 Plot the load line unto the transfer characteristic (4)

[TURN OVER]

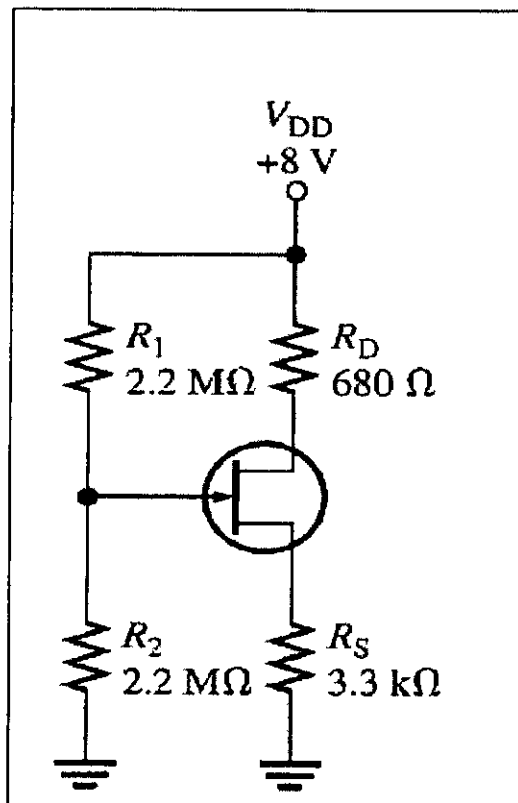


Figure 6

[14]

[TURN OVER]

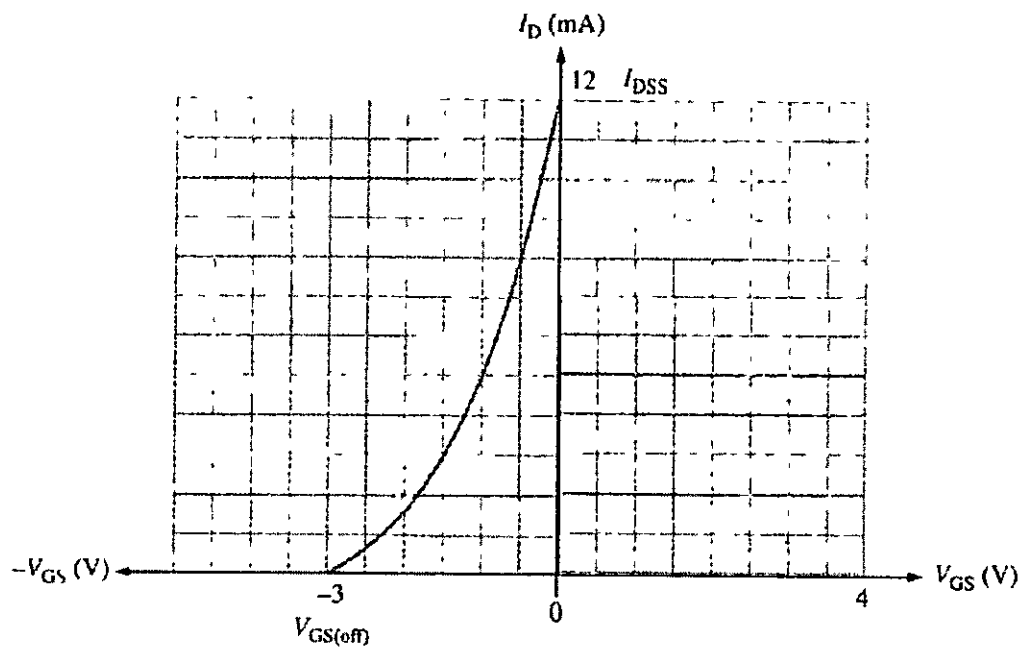


Figure 7

Question 9

True or False The JFET is always operated with the gate-source pn junction reverse biased

(2)

[2]

Total Marks [100]

Formula Sheet

$$V_{RIP(p-p)} = \left(\frac{V_{DC}}{2fCR_L} \right)$$

$$V_{RIP(p-p)} = \left(\frac{V_{DC}}{CfR_L} \right)$$

$$X_C = \frac{1}{2\pi fC}$$

$$V_{DC} = V_{pk} - \frac{1}{2}V_{RIP(p-p)}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}$$

$$V_{TH} = V_{CC} \left(\frac{R_{B2}}{R_{B1} + R_{B2}} \right)$$

$$\frac{V_{sec}}{V_{pri}} = \frac{N_{sec}}{N_{pri}}$$

$$\frac{I_{pri}}{I_{sec}} = \frac{N_{sec}}{N_{pri}}$$

$$r = \left(\frac{V_r}{V_{DC}} \right)$$

$$I_{B(min)} = \frac{I_{C(sat)}}{\beta_{DC}}$$

$$R_{TH} = \left(\frac{R_{B1} \times R_{B2}}{R_{B1} + R_{B2}} \right)$$

$$V_B \cong \left(\frac{R_2}{R_1 + R_2} \right) V_{CC}$$

$$A_v \cong \frac{R_C}{R_E}$$

$$A_v = \frac{R_C}{r'_e}$$

$$I_{ZM} = \frac{P_{D(max)}}{V_Z}$$

$$R_{in} = R_G \parallel \left(\frac{V_{GS}}{I_{GSS}} \right)$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$

$$V_B =$$

$$\left(\frac{R_2 \parallel \beta_{DC} R_E}{R_1 + (R_2 \parallel \beta_{DC} R_E)} \right) V_{CC}$$

$$V_r = \left(\frac{1}{fR_L C} \right) V_{p(rect)}$$

$$V_{DC} = \left(1 - \frac{1}{2fR_L C} \right) V_{p(rect)}$$

$$R_{surge} =$$

$$\frac{V_{p(sec)} - 1.4V}{I_{FSM}}$$

$$Z_Z = \frac{\Delta V_Z}{\Delta I_Z}$$

$$V_{AVG} = \frac{V_P}{\pi}$$

$$\beta_{DC} = \frac{\alpha_{DC}}{1 - \alpha_{DC}}$$

$$r'_c = \frac{h_{re} + 1}{h_{oe}}$$

$$r'_b = h_{ie} - \frac{h_{re}}{h_{oe}} (1 + h_{ie})$$

$$r'_e \cong \frac{25mV}{I_E}$$

$$A'_v = \left(\frac{V_b}{V_s} \right) A_v$$

$$A_v = \frac{R_C}{r'_e + R_E}$$

$$A_i = \frac{I_c}{I_s}$$

$$g_m = g_{m0} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)$$

$$g_{m0} = \frac{2I_{DSS}}{|V_{GS(off)}|}$$

$$R_{in} = \left| \frac{V_{GS}}{I_{GSS}} \right|$$

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD}$$

$$I_D = \frac{V_G - V_{GS}}{R_S}$$

$$A_v = \frac{V_{ds}}{V_{gs}}$$

$$R_S = \left| \frac{V_{GS}}{I_D} \right|$$

$$A_v = g_m \left(\frac{R_d r'_{ds}}{R_d + r'_{ds}} \right)$$

$$A_v = \frac{g_m R_d}{1 + g_m R_s}$$

$$I_D = \frac{I_{DSS}}{2}$$

$$I_D = \text{loss} \left(1 - \frac{I_D R_S}{V_{GS(off)}} \right)^2$$

$$f = \frac{1}{T}$$

$$A_{cl(M)} = 1 + \frac{R_f}{R_1}$$

$$V_{LTP} = \frac{R_2}{R_1 + R_2} (-V_{out(max)})$$

$$A_{cl(I)} = -\frac{R_f}{R_1}$$

$$V_{out} = -\left(\frac{V_C}{t} \right) R_f C$$

$$\frac{\Delta V_{out}}{\Delta t} = -\frac{V_{in}}{R_f C}$$

$$V_{UTP} = \frac{R_2}{R_1 + R_2} (+V_{out(max)})$$

$$F = \frac{kQ_1 Q_2}{d^2}$$

$$V_x = \left(\frac{C_T}{C_X} \right) V_S$$

$$L = \frac{N^2 \mu A}{l}$$

$$V_{OUT} = V_{REF} \left(1 + \frac{R_2}{R_1} \right) + I_{ADJ} R_2$$

$$L_M = k \sqrt{L_1 L_2}$$

$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \frac{1}{L_n}$$

$$\text{Percent load regulation} = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$

$$\text{Percent line regulation} = \frac{\Delta V_{OUT}}{\Delta V_{IN}} \times$$

100%

$$V_{OUT} = -\frac{R_f}{R} (V_{IN1} + V_{IN2} + \dots + V_{INn})$$

$$V_{OUT} = -\left(\frac{R_f}{R_1} V_{IN1} + \frac{R_f}{R_2} V_{IN2} + \dots + \frac{R_f}{R_n} V_{INn} \right)$$

$$\% \text{distortion}_{\text{NEW}} = \% \text{distortion}_{\text{ORIGINAL}} / [1 + (\beta * A)]$$

$$(\text{original}) / [1 + (\beta * A)]$$

$$Z_{\text{OUT}}(\text{new}) = Z_{\text{OUT}}$$

$$Z_{\text{OUT}}(\text{new}) = Z_{\text{OUT}}(\text{original}) * [1 + (\beta * A)]$$

$$[1 + (\beta * A)]$$

$$Z_{\text{IN}}(\text{new}) = Z_{\text{IN}}(\text{original}) *$$

$$Z_{\text{IN}}(\text{new}) = Z_{\text{IN}}(\text{original}) / [1 + (\beta * A)]$$

$$f_0 = 1 / [2\pi * \sqrt{L * C}]$$

$$\text{Modulation depth} = [(\text{signal peak}) / (\text{carrier peak})] * 100\%$$

$$\text{BW} = \text{LSB} + \text{USB}$$

$$A_d = -[(h_{fe} * R_C) / \{2 * (R_b + h_{ie})\}]$$

$$\text{BW}_{\text{NEW}} = \text{BW}_{\text{ORIGINAL}} + [1 + (\beta * A)]$$

$$A_v(\text{dB}) = A_{v1}(\text{dB}) + A_{v2}(\text{dB}) + \dots + A_{vn}(\text{dB})$$

$$A'_v = A_{v1} A_{v2} A_{v3} \dots A_{vn}$$

$$A_P = \beta_{\text{DC}} A_v$$

$$f_r = 1 / 2\pi \sqrt{LC}$$

$$V_{\text{DS}} = V_{\text{DD}} - I_{\text{DSS}} R_{\text{D}}$$

$$P_{\text{D(AVG)}}$$

$$P_{\text{out}} = V_{\text{rms(out)}} I_{\text{rms(out)}}$$

$$\text{eff} = P_{\text{OUT}} / P_{\text{OUT}} +$$

$$V_b = h_{ie} I_B$$

$$\beta = \beta_1 \beta_2$$

$$V_b = V_c h_{re}$$

$$I_c = I_b h_{fe}$$

$$I_c = V_c h_{oe}$$

$$h_{re} = h_{oe} r'_e$$

$$P_{\text{D(derated)}} = P_{\text{D(max)}} - (mW/C^\circ) \Delta T$$

$$R_1 // R_2 // R_{\text{IN(BASE)}}$$

$$R_{\text{in(base)}} = \beta_{ac} r'_e$$

$$R_{\text{in(to)}} =$$

$$R_{\text{in(base)}} = \beta_{ac} (r'_e + R_{E1})$$

$$A_p = A'_v A_i$$

$$A_v(\text{db}) = 20 \log A_v$$

$$V_{\text{GS}} = -I_D R_S$$

$$I_d = g_m V_{gs}$$

$$A_v = g_m R_d$$

$$V = I \times R$$

$$S = V \times I \times \cos \theta$$

$$\text{dB} = 10 \log A_p$$

$$V_{\text{OUT}} = -(V_{\text{IN1}} + V_{\text{IN2}} + \dots + V_{\text{Inn}})$$

$$A_{d(\text{VF})} = 1$$

$$V_{\text{HYS}} = V_{\text{UTP}} - V_{\text{ITP}}$$

$$V_{\text{DS}} = V_{\text{DD}} - I_{\text{DSS}} R_{\text{D}}$$

$$R_{\text{IN}} \cong \beta_{\text{DC}} R_{\text{E}}$$

$$V_{\text{GS}} = + I_D R_S$$

$$R_{\text{IN(base)}} \cong \beta_{\text{DC}} R_{\text{E}}$$

$$\text{TC} \times \Delta T$$

$$Q = 1,6 \times 10^{-19} C$$

$$\Delta V_z = V_z \times$$

$$R_{\text{in}} = R_1 // R_2 // R_{\text{IN(gate)}}$$

$$A_r = A / [1 + (\beta * A)]$$

$$Z_{\text{IN}} = h_{ie} + (h_{fe} + 1) * r_{e2}$$

$$F_0 = \sqrt{f_1 * f_2}$$

$$\text{BW} = f_2 - f_1$$

$$Q = f_0 / \text{BW}$$

$$f_0 = [1 / \{(2\pi)^2 * \sqrt{\{(1/L * C) - (R^2/L^2)\}}}]$$

$$Q = [\sqrt{L(C * R^2)}] - 1$$

$$R_p = (\omega_0^2 * L^2) / R_s$$

$$R_s = (\omega_0^2 * L^2) / R_p$$

$$Q = (1/R) * \sqrt{L/C}$$

$$Q_L = (\omega_0 * L) / R_x$$

$$Q_C = 1/(\omega_0 \cdot C)$$

$$R_0 = \sqrt{L/C}$$

$$f_c = 1/(\pi \cdot \sqrt{L \cdot C})$$

$$F_C = 1/4\pi \cdot \sqrt{L \cdot C}$$

$$C = C_N / (2\pi \cdot f_c \cdot R)$$

$$L = (R \cdot L_N) / (2\pi \cdot f_c)$$

$$A_0 = 3 - P$$

$$A_0 = (R_1 = R_2) / R_1$$

$$f_c = 1/(2\pi \cdot R \cdot C)$$

$$L = F \cdot N^2 \cdot D$$

$$F = \text{lower point} + (Z \cdot (X/Y))$$

$$Z_1 = Z' / (1 - A_V)$$

$$Z_2 = (Z' \cdot A_V) / (A_V - 1)$$

$$A_i = hf / [1 + (h_0 \cdot Z_L)]$$

$$A_V = (A / Z_i) \cdot Z_L$$

$$Z_i = h_i + (h_r \cdot A_i \cdot Z_L)$$

$$Y_0 = 1/Z_0 = h_0 - [(h_r \cdot h_r) / (h_i + R_s)]$$

$$V = IX_C$$

$$L_T = L_1 + L_2 + L_3 + \dots + L_n$$

$$X_L = 2\pi fL$$

$$V = IX_L$$

©

Unisa 2016