

**ECT2601  
RCT2601**

October/November 2017

**ELECTRONICS II (THEORY)**

Duration 3 Hours

100 Marks

**EXAMINERS**

FIRST

SECOND

MR PO UMENNE

MR NR NETSHIKWETA

**Programmable pocket calculator is permissible**

**Closed book examination**

**This examination question paper remains the property of the University of South Africa and may not be removed from the examination venue**

This examination question paper consists of 9 pages including this "cover" plus 3 pages formulae sheets

Answer all questions

PLEASE NOTE. IF YOU HAVE THE OPINION THAT INSUFFICIENT INFORMATION IS SUPPLIED FOR YOU TO ANSWER A PARTICULAR QUESTION, MAKE A REALISTIC ASSUMPTION, MOTIVATE IT AND THEN ANSWER THE QUESTION.

### BIPOLAR JUNCTION TRANSISTORS (BJT)

#### QUESTION 1

The transistor in figure 1 has the following maximum ratings  $P_{D(max)} = 700 \text{ mW}$ ,  $V_{CE(max)} 15 \text{ V}$ , and  $I_{C(max)} = 100 \text{ mA}$

- 1 1 Determine the maximum value to which  $V_{CC}$  can be adjusted without exceeding a rating (7)  
1 2 Which rating would be exceeded first? (5)

[12]

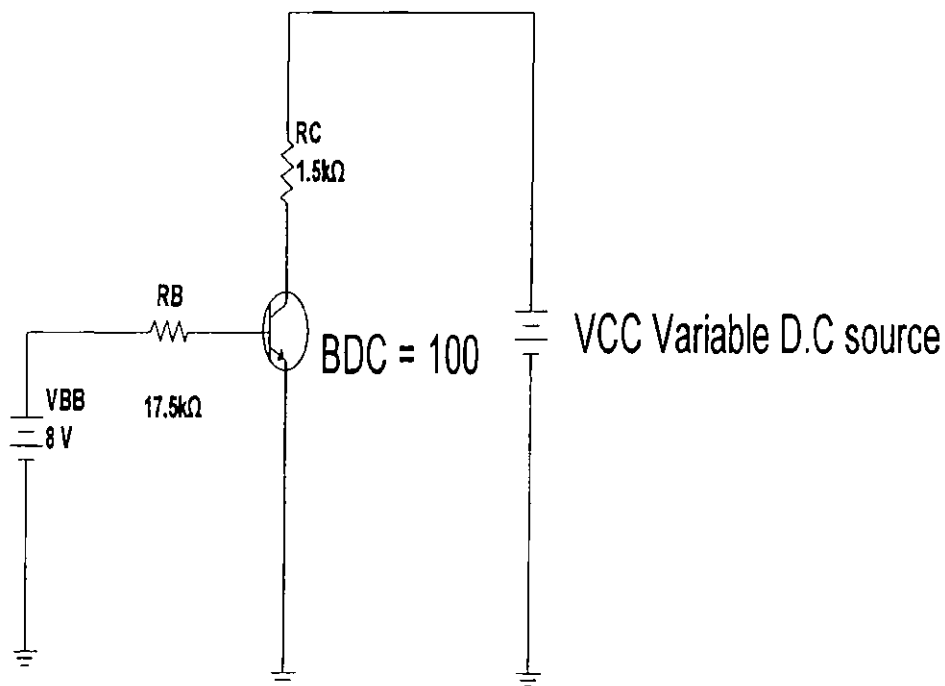


Figure 1

[TURN OVER]

## QUESTION 2

Determine whether or not the transistor in figure 2 is in saturation. Assume  $V_{CE(sat)} = 0.3\text{ V}$

(8)

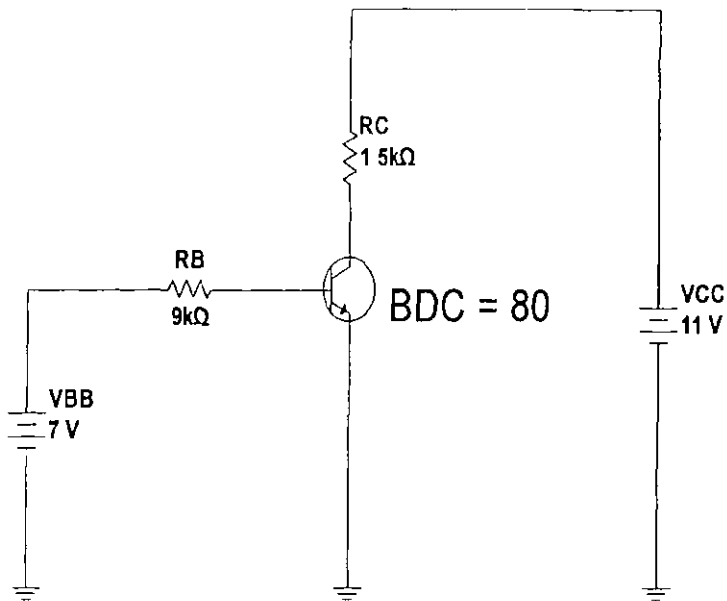
**[8]**

Figure 2

**[TURN OVER]**

TRANSISTOR BIAS CIRCUITS

## QUESTION 3

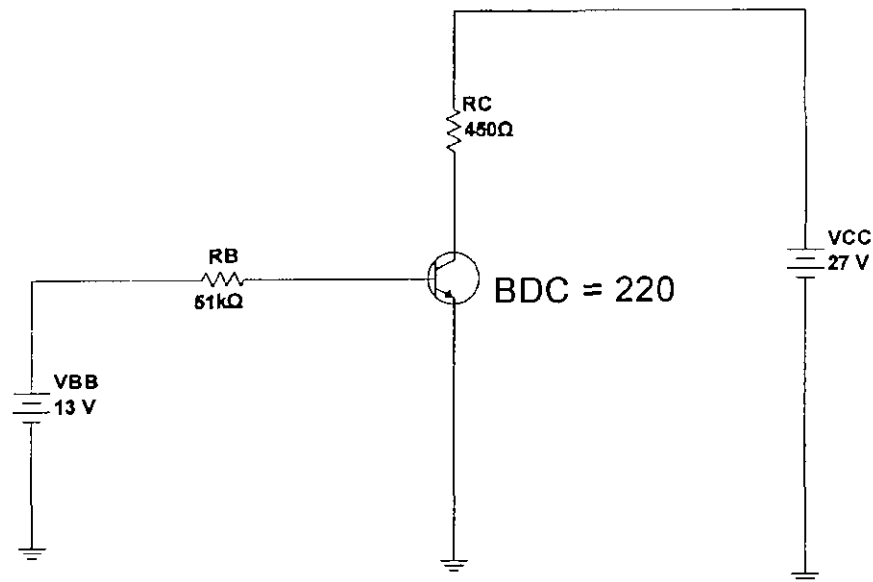


Figure 3

Determine the Q-point for the circuit above in figure 3

- 3 1 Calculate  $I_{CQ}$  and  $V_{CEQ}$  (6)
- 3 2 Find the maximum peak variation of the  $I_C$  (Assume  $V_{CE(SAT)} = 0.2 \text{ V}$ ) (4)
- 3 3 Calculate the maximum peak variation of the base current (2)

[12]

[TURN OVER]

**QUESTION 4**

For the transistor circuit in figure 4 calculate the following,

4.1  $I_C$  (6)

4.2  $V_{CE}$  (4)

**[10]**

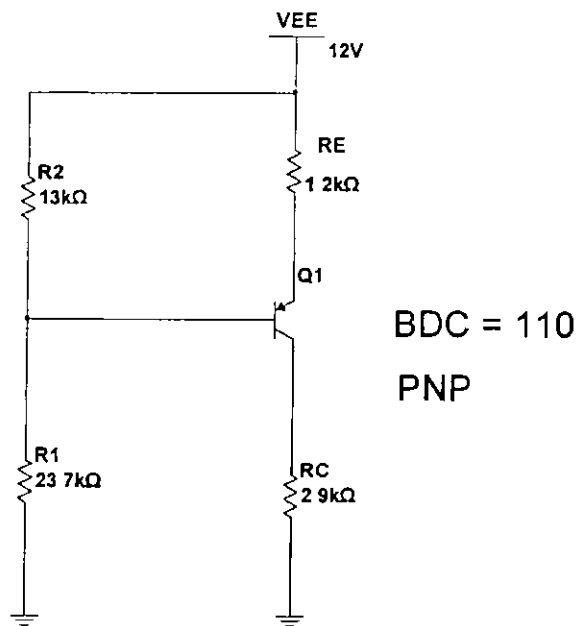


Figure 4

[TURN OVER]

## QUESTION 5

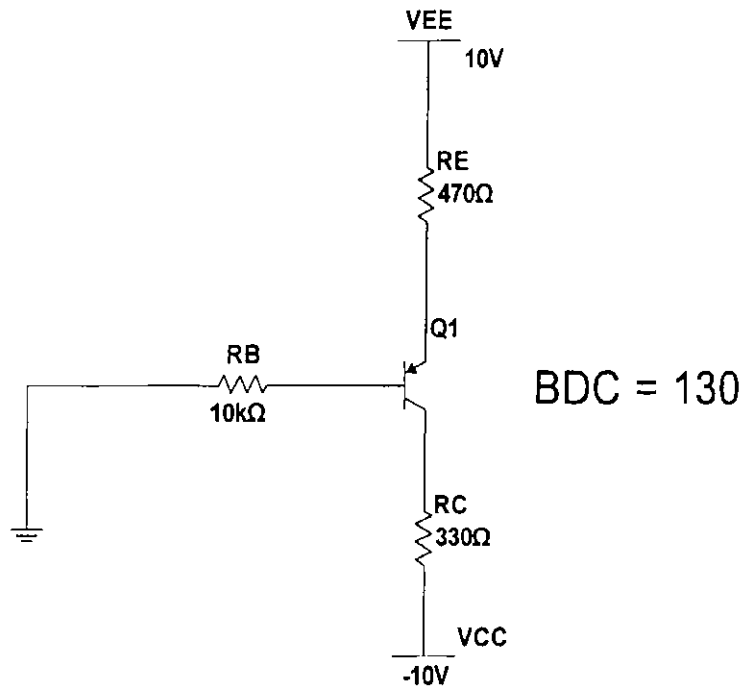


Figure 5

For the emitter bias circuit in figure 5 above

5 1 Calculate the  $I_E$  (4)

5 2 Calculate the  $V_{CE}$  (4)

**[8]**

**[TURN OVER]**

## BJT AMPLIFIERS

## QUESTION 6

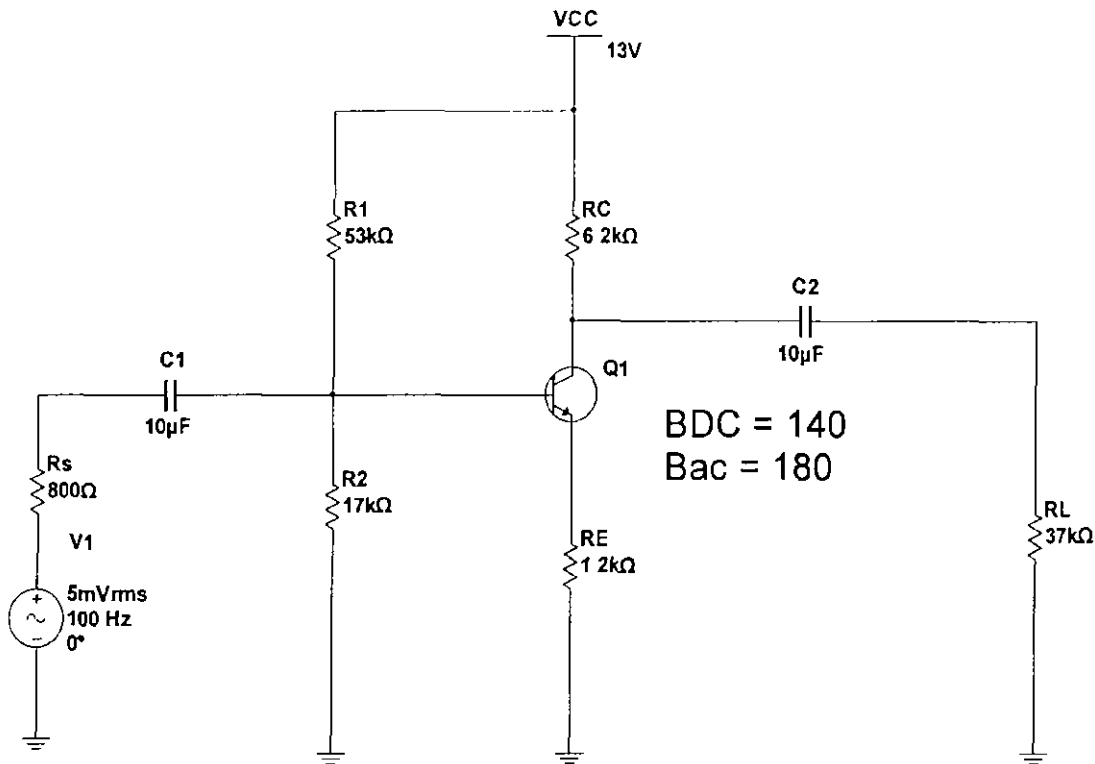


Figure 6

6 1 Determine all the d c values for the circuit in figure 6 above namely,

6 1 1  $I_E$  (6)

6 1 2  $V_E$  (2)

6 1 3  $V_B$  (2)

6.1 4  $V_C$  (2)

6 2 Determine all the a c values for the circuit in figure 6 above namely,

6.2 1  $r'_e$  (2)

6 2 2  $R_{in(base)}$  (2)

6 2 3  $R_{in(tot)}$  (2)

[TURN OVER]

- 6 2 4 Attenuation (2)
- 6 2 5 Gain ( $A_V$ ) (2)
- 6 2 6 Overall Gain (2)
- 6 2 7 ac collector voltage on the output (2)

**[26]****QUESTION 7**

For the common-base amplifier circuit in figure 7 below calculate,

- 7 1  $I_E$  (6)
- 7 2  $R_{in}$  (2)
- 7 3  $A_V$  (2)
- 7 4  $A_I$  (2)
- 7 5  $A_P$  (2)
- 7 6 output a c voltage if the input voltage is 1 mV as can be seen in figure 7 (2)

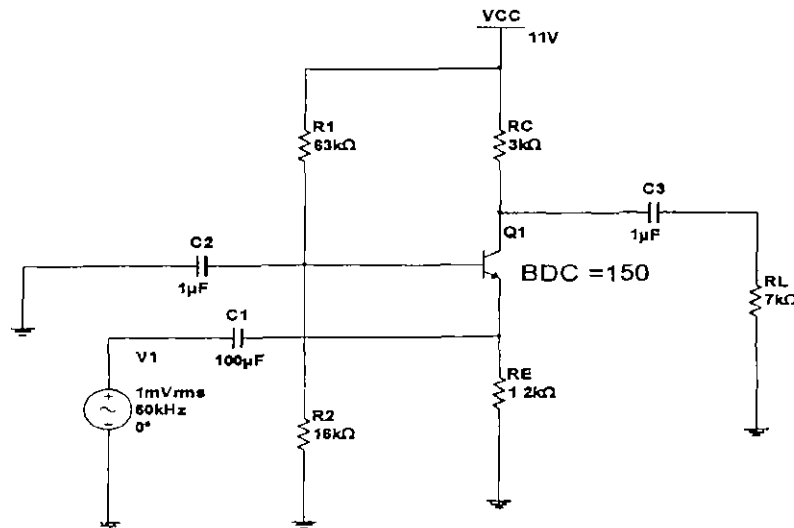
**[16]**

Figure 7

**[TURN OVER]**



## FIELD EFFECT TRANSISTORS

## QUESTION 8

For the JFET circuit in figure 8 below given that  $V_D$  calculate,

8.1  $I_D$  (4)

8.2  $V_{GS}$  (4)

**[8]**

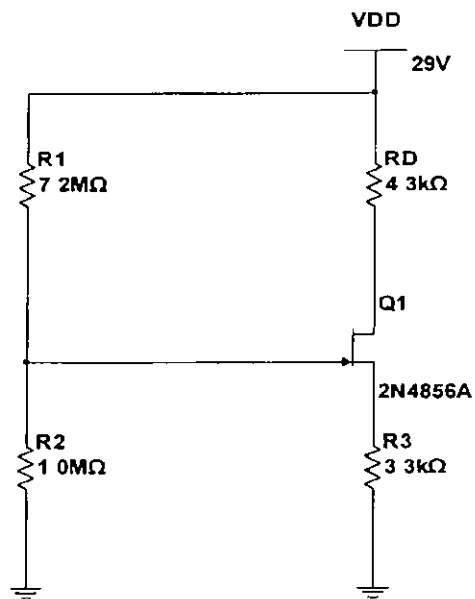


Figure 8

Total: 100

©

UNISA 2017

## Formula Sheet

$$V_{RIP(p-p)} = \left( \frac{V_{DC}}{2fCR_f} \right)$$

$$V_{RIP(p-p)} = \left( \frac{V_{DC}}{CfR_f} \right)$$

$$X_C = \frac{1}{2\pi fC}$$

$$V_{DC} = V_{pk} - \frac{1}{2}V_{RIP(p-p)}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_F}$$

$$V_{TH} = V_{CC} \left( \frac{R_{B2}}{R_{B1} + R_{B2}} \right)$$

$$\frac{V_{sec}}{V_{pri}} = \frac{N_{sec}}{N_{pri}}$$

$$\frac{I_{pri}}{I_{sec}} = \frac{N_{sec}}{N_{pri}}$$

$$r = \left( \frac{V_r}{V_{DC}} \right)$$

$$I_{B(min)} = \frac{I_{C(sat)}}{\beta_{DC}}$$

$$R_{TH} = \left( \frac{R_{B1} \times R_{B2}}{R_{B1} + R_{B2}} \right)$$

$$V_B \cong \left( \frac{R_2}{R_1 + R_2} \right) V_{CC}$$

$$A_v \cong \frac{R_C}{R_E}$$

$$A_v = \frac{R_C}{r'_c}$$

$$I_{ZM} = \frac{P_{D(max)}}{V_Z}$$

$$R_{in} = R_G \parallel \left( \frac{V_{GS}}{I_{GS}} \right)$$

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$

$$V_B = \left( \frac{R_2 \parallel \beta_{DC} R_E}{R_1 + (R_2 \parallel \beta_{DC} R_E)} \right) V_{CC}$$

$$V_r = \left( \frac{1}{fR_L C} \right) V_{p(rect)}$$

$$V_{DC} = \left( 1 - \frac{1}{2fR_L C} \right) V_{p(rect)}$$

$$R_{surge} = \frac{V_{p(sec)} - 1.4V}{I_{ISM}}$$

$$Z_Z = \frac{\Delta V_Z}{\Delta I_Z}$$

$$V_{AVG} = \frac{V_p}{\pi}$$

$$\beta_{DC} = \frac{\alpha_{DC}}{1 - \alpha_{DC}}$$

$$r'_c = \frac{h_{re} + 1}{h_{oe}}$$

$$r'_b = h_{ie} - \frac{h_{re}}{h_{oe}} (1 + h_{ie})$$

$$r'_e \cong \frac{25mV}{I_E}$$

$$A'_v = \left( \frac{V_b}{V_s} \right) A_v$$

$$A_v = \frac{R_C}{r'_e + R_E}$$

$$A_v = \frac{I_c}{I_r}$$

$$g_m = g_{m0} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)$$

$$g_{m0} = \frac{2I_{DSS}}{|V_{GS(off)}|}$$

$$R_{in} = \left| \frac{V_{GS}}{I_{GS}} \right|$$

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD}$$

$$I_D = \frac{V_G - V_{GS}}{R_S}$$

$$A_v = \frac{V_{ds}}{V_{gs}}$$

$$R_S = \left| \frac{V_{GS}}{I_D} \right|$$

$$A_v = g_m \left( \frac{R_d r'_{ds}}{R_d + r'_{ds}} \right)$$

$$A_v = \frac{g_m R_d}{1 + g_m R_s}$$

$$I_D = \frac{I_{DSS}}{2}$$

$$I_D = I_{DSS} \left( 1 - \frac{I_D R_S}{V_{GS(off)}} \right)^2$$

$$f = \frac{1}{T}$$

$$A_{cl(NI)} = 1 + \frac{R_f}{R_i}$$

$$V_{LIP} = \frac{R_2}{R_1 + R_2} (-V_{out(max)})$$

$$A_{cl(I)} = -\frac{R_f}{R_i}$$

$$V_{out} = -\left( \frac{V_C}{t} \right) R_f C$$

$$\frac{\Delta V_{out}}{\Delta t} = -\frac{V_m}{R_i C}$$

$$V_{UTP} = \frac{R_2}{R_1 + R_2} (+V_{out(max)})$$

$$F = \frac{k Q_1 Q_2}{d_2}$$

$$V_x = \left( \frac{C_T}{C_X} \right) V_S$$

$$L = \frac{N^2 \mu A}{I}$$

$$V_{OUT} = V_{R\&F} \left( 1 + \frac{R_2}{R_1} \right) + I_{ADJ} R_2$$

$$L_M = k \sqrt{L_1 L_2}$$

$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \frac{1}{L_n}$$

$$\text{Percent load regulation} = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$

$$\text{Percent line regulation} = \frac{\Delta V_{OUT}}{\Delta V_{IN}} \times 100\%$$

$$V_{OUT} = -\frac{R_f}{R} (V_{IN1} + V_{IN2} + \dots + V_{INn})$$

$$V_{OUT} = -\left( \frac{R_f}{R_1} V_{IN1} + \frac{R_f}{R_2} V_{IN2} + \dots + \frac{R_f}{R_n} V_{INn} \right)$$

$$\% \text{distortion}_{NEW} = \% \text{distortion}_{ORIGINAL} / [1 + (\beta^* A)]$$

$$Z_{OUT}(new) = Z_{OUT} (original) / [1 + (\beta^* A)]$$

$$Z_{OUT} (new) = Z_{OUT} (original) * [1 + (\beta^* A)]$$

$$Z_{IN} (new) = Z_{IN} (original) * [1 + (\beta^* A)]$$

$$Z_{IN} (new) = Z_{IN} (original) / [1 + (\beta^* A)]$$

$$f_0 = 1 / [2\pi * \sqrt{(L * C)}]$$

$$\text{Modulation depth} = [( \text{signal peak} ) / ( \text{carrier peak} )] * 100\%$$

$$BW = LSB + USB$$

$$A_d = -[(h_{fe} * R_C) / \{2 * (R_b + h_{ie})\}]$$

$$BW_{NEW} = BW_{ORIGINAL} + [1 + (\beta^* A)]$$

$$A_v(\text{dB}) = A_{v1}(\text{dB}) + A_{v2}(\text{dB}) + \dots + A_{vn}(\text{dB})$$

$$A'_v = A_{v1} A_{v2} A_{v3} \dots A_{vn}$$

$$A_p = \beta_{DC} A_v$$

$$f_r = 1 / 2\pi \sqrt{LC}$$

$$V_{DS} = V_{DD} - I_{DSS} R_D$$

$$P_{out} = V_{rms(out)} I_{rms(out)}$$

$$\text{eff} = P_{OUT} / P_{OUT} + P_{D(AVG)}$$

$$V_b = h_{ie} I_b$$

$$\beta = \beta_1 \beta_2$$

$$V_b = V_c h_{re}$$

$$I_c = I_b h_{fe}$$

$$I_c = V_c h_{oe}$$

$$h_{re} = h_{oe} r'_e$$

$$P_{D(\text{derated})} = P_{D(\text{max})} - (mW/C^\circ)\Delta T$$

$$R_{IN(\text{base})} = \beta_{ac}(r'_e + R_{E1})$$

$$V_{GS} = -I_D R_S$$

$$V = I \times R$$

$$V_{OUT} = -(V_{IN1} + V_{IN2} + \dots + V_{Inn})$$

$$V_{DS} = V_{DD} - I_{DSS} R_D$$

$$R_{IN(\text{base})} \cong \beta_{DC} R_E$$

$$R_{in} = R_1 \parallel R_2 \parallel R_{IN(\text{gate})}$$

$$f_0 = \sqrt{f_1 \cdot f_2}$$

$$f_0 = [1 / \{(2\pi) \cdot \sqrt{\{(1/L \cdot C) - (R^2/L^2)\}}]$$

$$R_s = (\omega \sigma^2 L^2) / R_p$$

$$Q_C = 1 / (\omega_0 \cdot C)$$

$$F_C = 1 / 4\pi \sqrt{L \cdot C}$$

$$A_0 = 3 - P$$

$$L = F \cdot N^2 \cdot D$$

$$Z_2 = (Z' \cdot A_v) / (A_v - 1)$$

$$Z_1 = h_i + (h_r \cdot A_i \cdot Z_L)$$

$$L_T = L_1 + L_2 + L_3 + \dots + L_n$$

$$R_{IN(\text{base})} = \beta_{ac} r'_e$$

$$A_p = A'_v A_i$$

$$I_d = g_m V_{gs}$$

$$S = V \times I \times \cos \theta$$

$$A_{cl(VF)} = 1$$

$$R_{IN} \cong \beta_{DC} R_E$$

$$Q = 1,6 \times 10^{-19} \text{ C}$$

$$A_r = A / [1 + (\beta \cdot A)]$$

$$BW = f_2 - f_1$$

$$Q = [\sqrt{L / (C \cdot R^2)}] - 1$$

$$Q = (1/R) \cdot \sqrt{L/C}$$

$$R_0 = \sqrt{L/C}$$

$$C = C_N / (2\pi \cdot f_C \cdot R)$$

$$A_0 = (R_1 = R_2) / R_1$$

$$F = \text{lower point} + (Z' \cdot (X/Y))$$

$$A_i = hf / [1 + (h_o \cdot Z_L)]$$

$$Y_0 = 1/Z_0 = h_o - [(h_r \cdot h_r) / (h_i + R_s)]$$

$$X_L = 2\pi f L$$

$$R_{IN(\text{tot})} = R_1 \parallel R_2 \parallel R_{IN(\text{BASE})}$$

$$A_v (\text{db}) = 20 \log A_v$$

$$A_v = g_m R_d$$

$$\text{dB} = 10 \log A_P$$

$$V_{HYS} = V_{UTP} - V_{ITP}$$

$$V_{GS} = + I_D R_S$$

$$\Delta V_Z = V_Z \times TC \times \Delta T$$

$$Z_{IN} = h_{ie} + (h_{fe} + 1) \cdot r_{e2}$$

$$Q = f_0 / BW$$

$$R_p = (\omega \sigma^2 L^2) / R_s$$

$$Q_L = (\omega \sigma L) / R_x$$

$$f_C = 1 / (\pi \sqrt{L \cdot C})$$

$$L = (R \cdot L_N) / (2\pi \cdot f_C)$$

$$f_C = 1 / (2\pi \cdot R \cdot C)$$

$$Z_1 = Z' / (1 - A_v)$$

$$A_v = (A_v / Z_i) \cdot Z_L$$

$$V = I X_C$$

$$V = I X_L$$