

## Assignment 2, Semester 2

### QUESTION 1

[40]

1.1 Convert the Hexadecimal number C6B to Octal. (6)

1.2 Convert the Binary number 1000101 to BCD. (6)

1.3 Draw the truth table of a 2 input NAND gate and draw the logic symbol of the NAND gate. (8)

1.4 Determine the 2's complement of 8 bit binary number 11111000 (4)

1.5 Develop a truth table for the standard SOP expression. (8)

$$X_{(ABC)} = (\bar{A}BC + AB\bar{C} + \bar{A}\bar{B}\bar{C})$$

1.6 Perform the following Addition (show all steps).

a.  $11110_2 + 10111_2$  (4)

b.  $67_8 + 54_8$  (4)

### QUESTION 2

[30]

2.1 Simplify the expression

$$\bar{W}X\bar{Y}\bar{Z} + \bar{W}XY\bar{Z} + WXYZ + W\bar{X}\bar{Y}\bar{Z} + W\bar{X}Y\bar{Z} + WX\bar{Y}Z + \bar{W}\bar{X}\bar{Y}Z + \bar{W}\bar{X}YZ$$

using a Karnaugh map. Please note: use WX in the rows and YZ in the columns. (14)

[TURN OVER]

2.2 Write the expanded forms of the terms in the given expression : (4)

$$F_{(ABCD)} = A B D + A C \bar{D}$$

2.3 Design the logic circuit for the expression

$$F_{(ABCD)} = \bar{A} \bar{B} C + A B C + \bar{A} B \bar{C} + A \bar{B} \bar{C} \quad (8)$$

2.4 Perform the Hexadecimal addition of two numbers (4)


$$9B_{16} \text{ and } F38_{16}$$

**QUESTION 3.** [30]

3.1 a. Convert the following Boolean expression into standard Product of Sum(POS) form.

$$X = (A+B+C)(\bar{A}+C+D)(A+\bar{B}+C+\bar{D}) \quad (6)$$

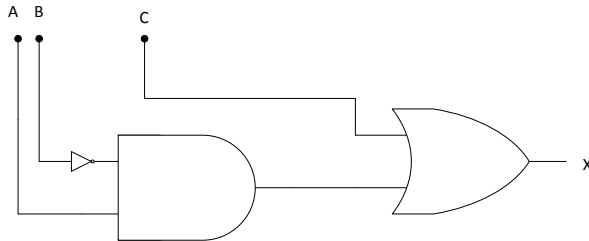b. Write the Boolean expression for the following logic circuit. (4)



3.2 a. Discuss the Positive edge triggered S-R flip flop and provide the logic symbol. (4)

b. Draw the truth table of a positive edge triggered S-R Flip flop. (6)

3.3 Apply Boolean Laws of Algebra to each one of the given expressions and simplify:

(a)  $X = \overline{(\bar{A} \bar{A} \bar{B})} C$  (5)

(b)  $X = A(B + C + \overline{\bar{D} + \bar{E}}) E$  (5)